

Relay Switch Circuit

Relays are electromechanical devices that use an electromagnet to operate a pair of movable contacts from an open position to a closed position.

The advantage of relays is that it takes a relatively small amount of power to operate the relay coil, but the relay itself can be used to control motors, heaters, lamps or AC circuits which themselves can draw a lot more electrical power.

The electro-mechanical relay is an output device (actuator) which come in a whole host of shapes, sizes and designs, and have many uses and applications in electronic circuits. But while electrical relays can be used to allow low power electronic or computer type circuits to switch relatively high currents or voltages both “ON” or “OFF”, some form of **relay switch circuit** is required to control it.

The design and types of relay switching circuits is huge, but many small electronic projects use transistors and MOSFETs as their main switching device as the transistor can provide fast DC switching (ON-OFF) control of the relay coil from a variety of input sources so here is a small collection of some of the more common ways of switching relays.


NPN Relay Switch Circuit

A typical relay switch circuit has the coil driven by a NPN transistor switch, TR₁ as shown depending on the input voltage level. When the Base voltage of the transistor is zero (or negative), the transistor is cut-off and acts as an open switch. In this condition no Collector current flows and the relay coil is de-energised because being current devices, if no current flows into the Base, then no current will flow through the relay coil.

If a large enough positive current is now driven into the Base to saturate the NPN transistor, the current flowing from Base to Emitter (B to E) controls the larger relay coil current flowing through the transistor from the Collector to Emitter.

For most bipolar switching transistors, the amount of relay coil current flowing into the Collector would be somewhere between 50 to 800 times that of the required Base current to drive the transistor into saturation. The current gain, or beta value (β) of the general purpose BC109 shown is typically about 290 at 2mA (Datasheet).

NPN Relay Switch Circuit

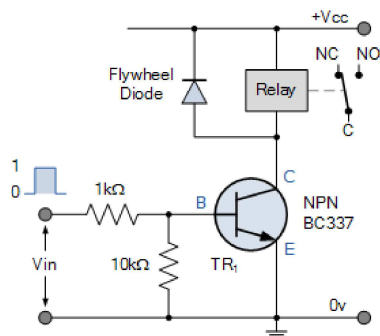

Note that the relay coil is not only an electromagnet but it is also an inductor. When power is applied to the coil due to the switching action of the transistor, a maximum current will flow as a result of the DC resistance of the coil as defined by Ohms Law, ($I = V/R$). Some of this electrical energy is stored within the relay coil's magnetic field.

When the transistor switches "OFF", the current flowing through the relay coil decreases and the magnetic field collapses. However the stored energy within the magnetic field has to go some where and a reverse voltage is developed across the coil as it tries to maintain the current in the relay coil. This action produces a high voltage spike across the relays coil that can damage the switching NPN transistor if allowed to build up.

So in order to prevent damage to the semiconductor transistor, a "flywheel diode", also known as a freewheeling diode, is connected across the relay coil. This flywheel diode clamps the reverse voltage across the coil to about 0.7V dissipating the stored energy and protecting the switching transistor. Flywheel diodes are only applicable when the supply is a polarized DC voltage. An AC coil requires a different protection method, and for this an RC snubber circuit is used.


NPN Darlington Relay Switch Circuit

The previous NPN transistor relay switch circuit is ideal for switching small loads such as LED's and miniature relays. But sometimes it is required to switch larger relay coils or currents beyond the range of a BC109 general purpose transistor and this can be achieved using **Darlington Transistors**.

The sensitivity and current gain of a relay switch circuit can be greatly increased by using a Darlington pair of transistors in place of a single switching transistor. Darlington Transistor pairs can be made from two individually connected Bipolar Transistors as shown or available as one single device with standard: Base, Emitter and Collector connecting leads.

The two NPN transistors are connected as shown so that the Collector current of the first transistor, TR₁ becomes the Base current of the second transistor TR₂. The application of a positive base current to TR₁ automatically turns "ON" the switching transistor, TR₂.

NPN Darlington Relay Switch Circuit

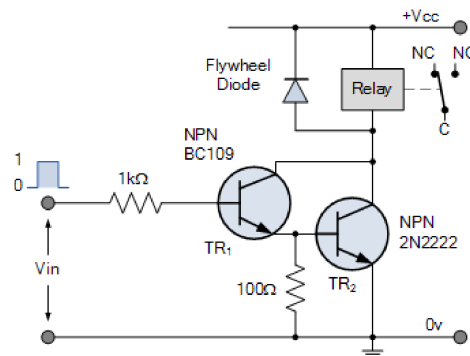


If two individual transistors are configured as a Darlington switching pair, then a small value resistor (100 to 1,000Ω's) is usually placed between the Base and Emitter of the main switching transistor, TR₂ to ensure that it turns fully OFF. Again a flywheel diode is used to protect TR₂ from the back emf generated when the relay coil is de-energised.

Emitter Follower Relay Switch Circuit

As well as the standard Common Emitter configuration for a relay switch circuit, the relay coil can also be connected to the Emitter terminal of the transistor to form an Emitter Follower circuit. The input signal is connected directly to the Base, while the output is taken from the Emitter load as shown.

Emitter Follower Relay Switch Circuit

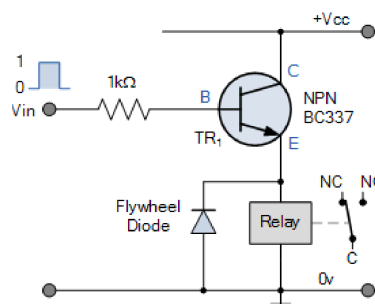


The Common Collector, or Emitter Follower configuration is very useful for impedance matching applications because of the very high input impedance, in the region of hundreds of thousands of Ohms while having a relatively low output impedance to switch the relays coil. As with the previous NPN relay switch circuit, switching occurs by applying a positive current to the base of the transistor.

Emitter Darlington Relay Switch Circuit

This is the Darlington transistor version of the previous Emitter Follower circuit. A very small positive Base current applied to TR1 causes a much greater Collector current to flow through TR2 due to the multiplication of the two Beta values.

Emitter Darlington Relay Switch Circuit

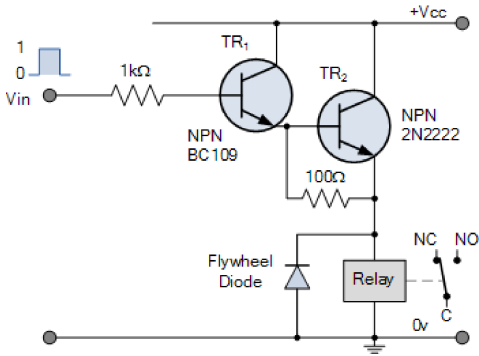


The Common Emitter Darlington relay switch circuit is useful to provide current gain and power gain with the voltage gain approximately equal to unity. Another important characteristic of this type of Emitter Follower circuit is that it has a high input impedance and a low output impedance, which make it ideal for impedance matching to large relay coils.

PNP Relay Switch Circuit

As well as switching relay coils and other such loads with **NPN Bipolar Transistors**, we can also switch them using **PNP Bipolar Transistors**. The PNP relay switch circuit is no different to the NPN relay switching circuit in terms of its ability to control the relays coil. However, it does require different polarities of operating voltages. For example, the Collector–Emitter voltage, V_{ce} , must be negative for the PNP type to cause current flow from the Emitter to the Collector.

PNP Relay Switch Circuit

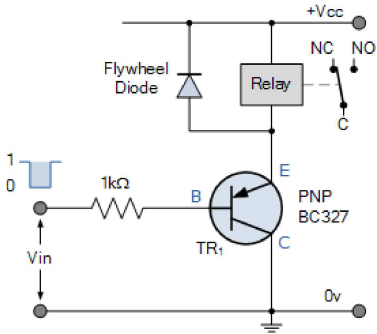

The PNP transistor circuit works in opposite to the NPN relay switching circuit. Load current flows from the Emitter to the Collector when the Base is forward biased with a voltage that is more negative than that at the Emitter. For the relays load current to flow through the Emitter to the Collector, both the Base and the Collector must be negative in respect to the Emitter.


In other words, when Vin is HIGH the PNP transistor is switched “OFF” and so too is the relay coil. When Vin is LOW, the Base voltage is less than the Emitter voltage, (more negative) and the PNP transistor turns “ON”. The Base resistor value sets the Base current, which sets the Collector current that drives the relay coil.

PNP transistor switches can be used when the switching signal is the reverse for an NPN transistor, for example the output of a CMOS NAND gate or other such logic device. A CMOS logic output has the drive strength at logic 0 to sink sufficient current to turn the PNP transistor “ON”. Then current sinks can be turned into current sources by using PNP transistors and a power supply of opposite polarity.

PNP Collector Relay Switch Circuit

The operation of this circuit is the same as the previous relay switching circuit. In this relay switch circuit, the relay load has been connected to the PNP transistors Collector. The ON–OFF switching action of the transistor and coil occurs when Vin is LOW, transistor “ON” and when Vin is HIGH, transistor “OFF”.

PNP Collector Relay Switch Circuit

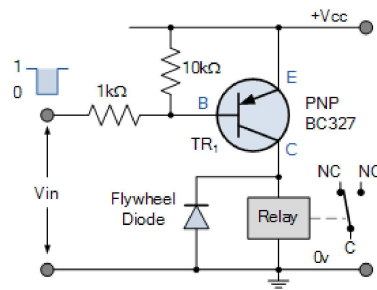

We have seen that either an NPN bipolar transistor or an PNP bipolar transistor can operate as a switch for relay switching, or any other load for that matter. But that there are two different conditions that need to be understood as the current flows in two different directions.

So in an NPN transistor, a HIGH voltage with respect to the Emitter is applied to the Base, current flows from the Collector to the Emitter and the NPN transistor switches “ON”. For a PNP transistor, a LOW voltage with respect to the Emitter is applied to the Base, current flows from the Emitter to the Collector and the PNP transistor switches “ON”.


N-channel MOSFET Relay Switch Circuit

MOSFET relay switching operation is very similar to Bipolar Junction Transistor (BJT) switch operation seen above, and any of the previous circuits can be implemented using MOSFETs. However, there are some major differences in the operation of the MOSFET circuits with the main ones being that MOSFETs are voltage operated devices, and as the Gate is electrically isolated from the Drain-Source channel, they have very high input impedances so the Gate current for a MOSFET is zero, therefore a base resistor is unnecessary.

MOSFETs conduct through a conductive channel with the channel initially being closed, transistor “OFF”. This channel gradually increasing in conductive width as the voltage applied to the Gate terminal is slowly increased. In other words, the transistor operates by enhancing the channel as the Gate voltage increases and for this reason the this type of MOSFET is called an Enhancement MOSFET, or E-MOSFET.

N-channel Enhancement MOSFETs (NMOS) are the most commonly used type of MOSFET as a positive voltage on the Gate terminal switches the MOSFET “ON” and zero or a negative voltage on the Gate switches it “OFF”, making ideal as MOSFET relay switch. Complementary P-channel Enhancement MOSFETs are also available which, like the PNP BJT work with opposite voltages.

N-channel MOSFET Relay Switch Circuit

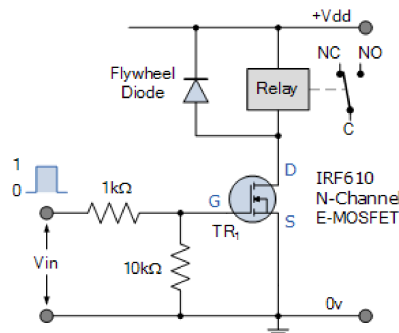


The above MOSFET relay switch circuit is connected in a common-source configuration. With zero voltage input, LOW condition, the value of V_{GS} , there is insufficient Gate drive to open the channel and the transistor is “OFF”. But when V_{GS} is increased above the MOSFETs lower threshold voltage V_T , the channel opens, current flows and the relay coil is operated.

Then the enhancement mode MOSFET operates as a normally open switch making it ideal for switching small loads such as relays. E-type MOSFETs have high “OFF” resistance but moderate “ON” resistance (OK for most applications), so when selecting one for a particular switching application, its R_{DS} value needs to be taken into consideration.

P-channel MOSFET Relay Switch Circuit

The P-channel Enhancement MOSFET (PMOS) is constructed the same as for the N-channel Enhancement MOSFET except that it operates with negative Gate voltages only. In other words, A P-channel MOSFET operates in the same fashion but with opposite polarities as the Gate must be more negative than the Source to turn “ON” the transistor by being forward-biased as shown.

P-channel MOSFET Relay Switch Circuit

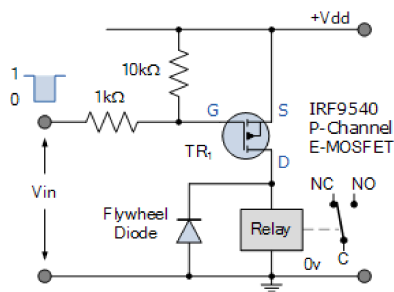

In this configuration, the P-channels Source terminal is connected to +Vdd and the Drain terminal is connected to ground via the relays coil. When a HIGH voltage level is applied to the Gate, the P-channel MOSFET will be turned “OFF”. The turned “OFF” E-MOSFET will have a very high channel resistance and acts nearly like an open circuit.


When a LOW voltage level is applied to the Gate, the P-channel MOSFET will be turned “ON”. This will cause current to flow through the low resistance path of e-MOSFETs channel operating the relay coil. Both N-channel and P-channel e-MOSFETs make excellent low voltage relay switching circuits and can easily be interfaced to a wide variety of digital logic gates and micro-processor applications.

Logic Controlled Relay Switch Circuit

The N-channel, enhancement-type MOSFET is extremely useful as a transistor switch because in its “OFF” state (with zero Gate bias) its channel has a very high resistance blocking current flow. However, a relatively small positive voltage greater than the threshold voltage V_T , on its high impedance Gate causes it to begin conducting current from its Drain terminal to its Source terminal.

Unlike the Bipolar Junction Transistor which requires a Base current to turn it “ON”, the e-MOSFET only requires a voltage on the Gate as due to its insulated Gate construction, zero current flows into the Gate. Then this makes the e-MOSFET, either N-channel or P-channel ideal to be driven directly by typical TTL or CMOS logic gates as shown.

Logic Controlled Relay Switch Circuit

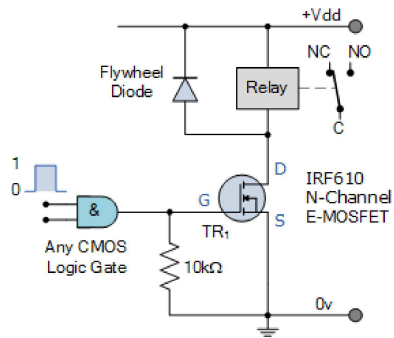


Here the N-channel E-MOSFET is being driven by a digital logic gate. The output pins of most logic gates can only supply a limited amount of current, typically no more than about 20 mA. As e-MOSFETs are voltage operated devices and consume no Gate current, we can use a MOSFET relay switch circuit to control high power loads.

Micro-controller Relay Switch Circuit

As well as digital logic gates, we can also use the output pins and channels of micro-controllers, PIC’s and processors to control the outside world. The circuit below shows how to interface a relay using a MOSFET switch.

Micro-controller Relay Switch Circuit

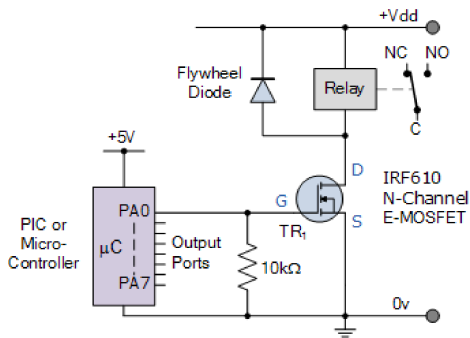

Relay Switching Circuit Summary

In this tutorial we have seen how we can use both Bipolar Junction Transistors, either NPN or PNP and Enhancement MOSFETs, either N-channel or P-channel as a transistor switching circuit.

Sometimes when building Electronic or Micro-controller circuits we want to use a transistor switch to control a high-power device, such as motors, lamps, heating elements or AC circuits. Generally these devices require larger currents or higher voltages than a single power transistor can handle then we can use a relay switching circuit to do this.

Bipolar transistors (BJT’s) make very good and cheap relay switching circuits, but BJT’s are current operated devices as they convert a small Base current into a larger load current to energise the relay coil.

However, the MOSFET switch is ideal as an electrical switch as it takes virtually no Gate current to turn “ON”, converting a Gate voltage into a load current. Therefore, a MOSFET can be operated as a voltage-controlled switch.

In many applications bipolar transistors can be substituted with enhancement-type MOSFETs offering faster switching action, much higher input impedance, and probably less power dissipation. The combination of a very high Gate impedance, very low power consumption in its “OFF” state, and very fast switching capability makes the MOSFET suitable for many digital switching applications. Also with zero Gate current its switching action can not overload the output circuit of a digital gate or micro-controller.

However, because the gate of an E-MOSFET is insulated from the rest of the component, it is especially sensitive to static electricity which could destroy the thin oxide layer on the Gate. Then special care should be taken either when handling the component, or when it is in use and that any circuit using e-MOSFETs includes appropriate protection from static and voltage spikes.

Also for additional protection of either BJT’s or MOSFETs, always use a flywheel diode across and relay coil to safely dissipate the back emf generated by the transistors switching action.

38 Comments

Join the conversation!

Your Name

Email Address

Write your comment here

SUBMIT

A Anand

Thank you for the information.
So which is best circuit above to turn the electrical switch of 230v single phase motor turn on and rigid, based on the detection by a water sensor. Thank you.

Posted on March 11th 2017 | 5:18 pm

⬅️ Reply

kuldeep sharma

Please tell me single phase solid state relay circuit diagram

Posted on March 02nd 2017 | 4:37 pm

↩ Reply



Wayne Storr

Please use the site, instead of posting these sorts of questions. Solid State Relay

Posted on March 02nd 2017 | 5:37 pm

↩ Reply



Owen

In the case of dialinton pair,why the transistors are not the same number, eg, 2N2222* 2 ?

Posted on February 11th 2017 | 7:19 am

↩ Reply



Wayne Storr

Both transistors could be the same, but would be a waste of a transistor. In a Darlington pair, one transistor is the low power switching transistor and the other is the high power current carrying transistor.

Posted on February 11th 2017 | 7:25 am

↩ Reply

O Ott

But what about analog switches? It seems that analog switches use less power. I need to switch 20 small (audio) relays which nominal operating power is 11,7mA (12V), so they do not need much power to operate.

Any thoughts?

Posted on February 04th 2017 | 2:19 pm

↩ Reply

O Ott

Thank You!

Posted on January 31st 2017 | 1:09 pm

↩ Reply

H Hasan Yahya

It seem that this article is still difficult to be understood, especially for a beginner, if ” Relay” showed as a rectangular box. How it work, consist of what component, and material is, can constitute the questions. Thank in advance to author.

Posted on August 05th 2016 | 2:42 pm

↩ Reply

C Craig Bowman

I wonder if the world would be different?
I am asked to draw the pcb lines drawing for a computer controlled Relay, we had the circuit diagram for.
This is just after, I think, I had to run a new ethernet cable along basement corridors for a University. This was year ten work experience. This was 1986.
Unfortunately, I had not done the relay assignment. I would have to perform better.
My question is now, may this task have been an important cofactor to the ethernet cable lay out or not? Is computer communication technology so acute and balanced that I may research a physical relay switch a missing part and without it something may have gone viral in my personal biophysical chemistry after years of consumption of the powerful networked computers by the University users. Or is this too esoteric? Or and again is this my stand alone intelligence and youthfulness that recalls a missed piece of work and stretch of brain power and the thanks from what may have been an achievement?
Yours Kindly, Craig.

Posted on July 08th 2016 | 6:24 pm

[↩ Reply](#)

A Ash

Cool

Posted on June 21st 2016 | 8:07 am

[↩ Reply](#)

m mighty igor

I want to know which kind of relay Im going to use in designing automatic phase change over switch

Posted on June 18th 2016 | 6:50 am

[↩ Reply](#)

N Nayyar

I want to design a relay switching system to be operated remotely through hard wire from 30 different locations (flats of a residential multi- storied building) to operate a centralized entry door fitted with 6V DC magnetic lock. need advice.

Posted on May 12th 2016 | 5:37 pm

[↩ Reply](#)

More

View More

THE BASICS

- Contact Us
- Privacy Policy
- Terms of Use
- Feedback

FOR ADVERTISERS

- Contact Sales
- Media Guide Request

ASPENCORE NETWORK

[ElectroSchematics](#)

[Electronic Products](#)

[ICC Media](#)

[EEWeb](#)

[Engineers Garage](#)

[Electronics Tutorials](#)

[Embedded Developer](#)


[Elektroda](#)

[Mikrocontroller](#)

[EEM](#)

CONNECT WITH US

 [Facebook](#)

 [Google+](#)

